

Altair Manual Part 1 notes

Saturday, August 30, 2025 1:26 PM

Part 1: Introduction

- Altair 8800 has 78 machine language instructions
- You can learn how to use it even if you have little to no knowledge if you read this manual

A. Logic

- George Boyle a nineteenth century British mathematician made a detailed study of the relationship between certain fundamental logic and expressions and their arithmetic counter parts
- His logic is frequently called Boolean Algebra
- Boolean: True or false
- Can't be both or partially true and partially false
- ON = true
- OFF = false
- An electronic analogy of a logical statement can be readily synthesized
- Three basic logic statements:
 - And: TRUE if all of its logic condition are true
 - Or: TRUE if any of its logic conditions is true
 - Not: Just flip flops; A true statement is false and a false statement is true
- OFF = 0
- ON = 1

Conditions (Inputs)	Conclusion (outputs)
False And False	False
False And True	False
True And False	False
True And True	True

Electronic ON-OFF switch equivalent

Conditions (off-on)	Conclusion (output)
0 - 0	0
0 - 1	0
1 - 0	0
1 - 1	1

Numerical equivalents

Conditions (Inputs)	Conclusion (outputs)
0 AND 0	0
0 AND 1	0
1 AND 0	0
1 AND 1	1

Truth table

And		OR		Not	
A	B	out	A	B	out
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	1	1	0

B. Electronic Logic

- 3 basic logic functions can be used by a simple transistor circuits

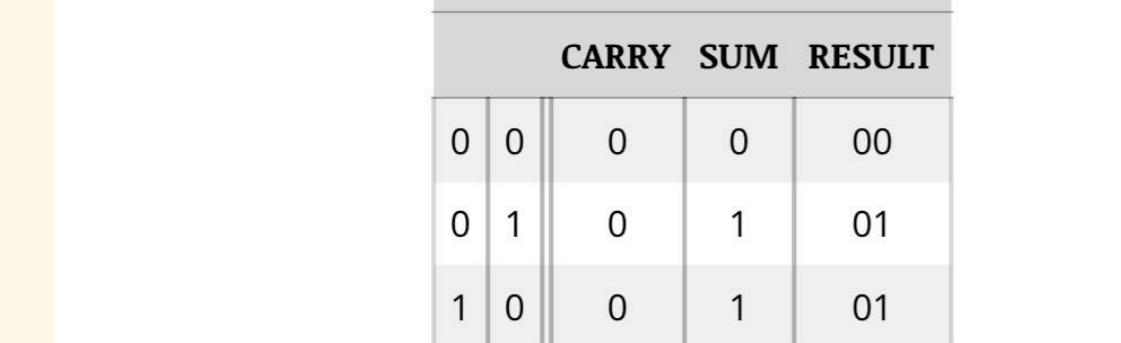


FIGURE 1-4. The Three Main Logic Symbols

AND		OR		NOT	
A	B	OUT	A	B	OUT
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	1	1	0

- Three basic logic circuits can be combined to produce more logic analogies such as NAND (NOT-AND) and NOR (NOT-OR).


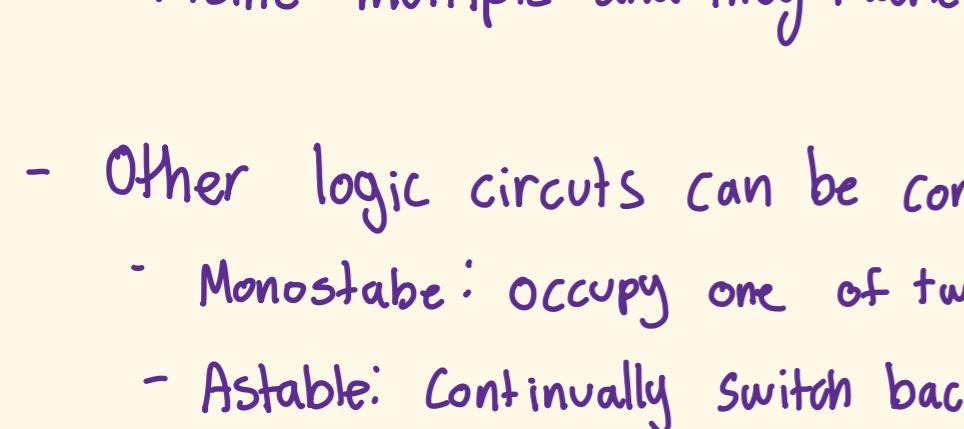


FIGURE 1-5. The NAND and NOR Circuits

NAND			NOR		
A	B	OUT	A	B	OUT
0	0	1	0	0	1
0	1	1	0	1	0
1	0	1	1	0	0
1	1	0	1	1	0

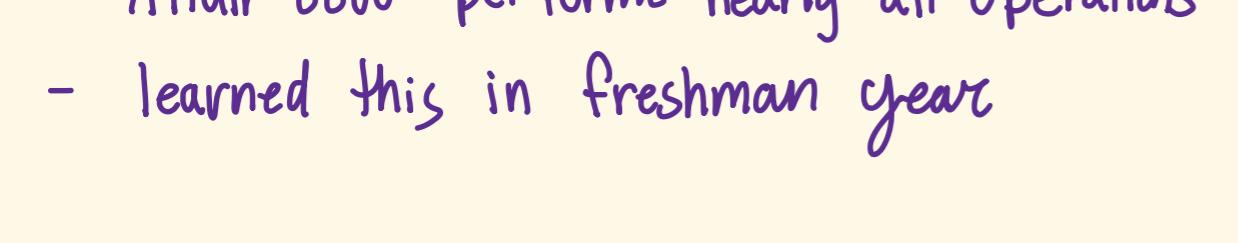- Three or more logic circuits make a logic system
- Most basic logic systems is the EXCLUSIVE OR circuit



A	B	A and B	not (A and B)	A or B	(not (A and B)) and (A or B)
0	0	0	1	0	0
0	1	0	1	1	1
1	0	0	1	1	1
1	1	1	0	1	0

- EXCLUSIVE-OR circuit can be used to implement logical functions and it can be used to add two or more input conditions

- Compatible with the binary number system

- Often called a binary adder

A	B	CARRY	OUT a.k.a. SUM
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- EXCLUSIVE-OR circuit can be used to implement logical functions and it can be used to add two or more input conditions

- Compatible with the binary number system

- Often called a binary adder

A	B	CARRY	SUM
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- EXCLUSIVE-OR circuit can be used to implement logical functions and it can be used to add two or more input conditions

- Compatible with the binary number system

- Often called a binary adder

A	B	CARRY	RESULT
0	0	0	00
0	1	0	01
1	0	0	01
1	1	1	10

- EXCLUSIVE-OR circuit can be used to implement logical functions and it can be used to add two or more input conditions

- Compatible with the binary number system

- Often called a binary adder

A	B	CARRY	OUT
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- EXCLUSIVE-OR circuit can be used to implement logical functions and it can be used to add two or more input conditions

- Compatible with the binary number system

- Often called a binary adder

A	B	CARRY	OUT
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

- EXCLUSIVE-OR circuit can be used to implement logical functions and it can be used to add two or more input conditions